
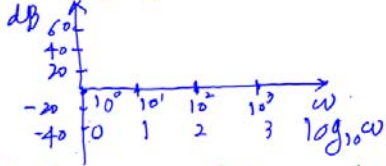


Bode plot

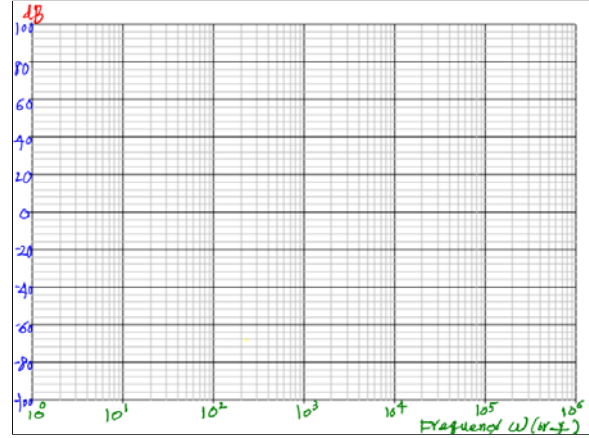

Recall $\log_{10} A \cdot B = \log_{10} A + \log_{10} B$
 $\log_{10} \frac{A}{B} = \log_{10} A - \log_{10} B$




ECE 103L #6 Filter Design

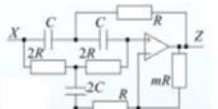1. In the lab we analyzed filtering 60 Hz power-line noise from ECG signal using a digital (signal processing) filter. Now let's try to an analog (circuit) filter approach to remove the 60 Hz line-noise. Following is an active twin-T notch filter with transfer function:



$$H(\omega) = \frac{Z(\omega)}{X(\omega)} = \frac{(1+m)(2j\omega RC)^2 + 1}{(2j\omega RC)^2 + 4(1-m)j\omega RC + 1}$$

Here m is the ratio of the two feedback resistances which determines the gain and quality for the filter. The drop frequency of this twin-T notch filter is $f_{drop} = 1/4\pi RC$. For designing a 60 Hz drop filter, let's use $R=10 \text{ k}\Omega$ and $C=133 \text{ nF}$.



$H(\omega) = 0$ when $(2j\omega RC)^2 = -1$
 $(2\omega RC)^2 = 1 \Rightarrow \omega = \frac{1}{2RC} = \frac{1}{4\pi RC}$

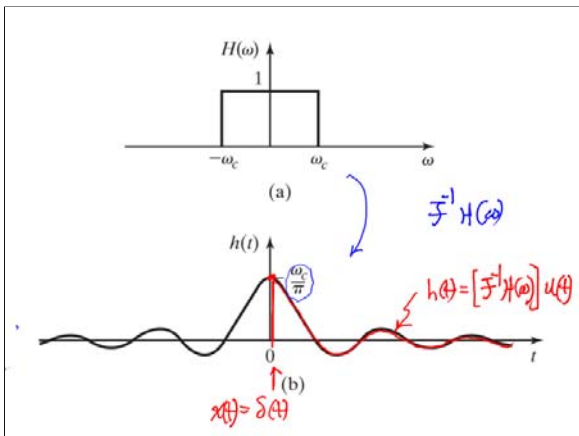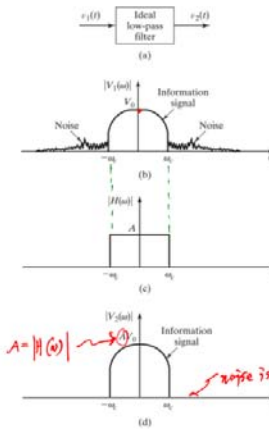- (a) For $m = \{0.8, 0.9\}$ plot the magnitude and phase response of $H(\omega)$ with a range of $f = \omega/2\pi = [0, 200 \text{ Hz}]$.
- (b) Consider the ECG signal used during the class (ecg_signal.mat) as the input ($x(t) = \text{ecg}$) of a 60 Hz twin-T notch filter with $m=0.9$. Using the functions `fft()` and `ifft()`, determine the $X(\omega)$, $Z(\omega)$, and $z(t)$ in a 4x1 subplot for the range of $-250 \leq f \leq 250$ and $0 \leq t \leq 2.5$.



$$h(t) = \frac{1}{2\pi} \int_{-\omega_c}^{\omega_c} H(\omega) e^{-j\omega t} d\omega$$

$$= \frac{1}{2\pi} \int_{-\omega_c}^{\omega_c} 1 e^{-j\omega t} d\omega = \frac{1}{2\pi} \left[\frac{e^{-j\omega t}}{-jt} \right]_{-\omega_c}^{\omega_c}$$







$$= \frac{1}{2\pi} \frac{1}{jt} \left[e^{-j\omega_c t} - e^{-j(-\omega_c)t} \right]$$

$$= \frac{1}{2\pi} \frac{1}{jt} \left[e^{-j\omega_c t} - e^{j\omega_c t} \right]$$

$$= \frac{1}{2\pi} \frac{1}{jt} \left[\frac{j\omega_c t - j\omega_c t}{2j} \right]$$

$$= \frac{1}{\pi} \left[\frac{j\omega_c t - j\omega_c t}{2j} \right] \frac{\omega_c}{\omega_c t}$$
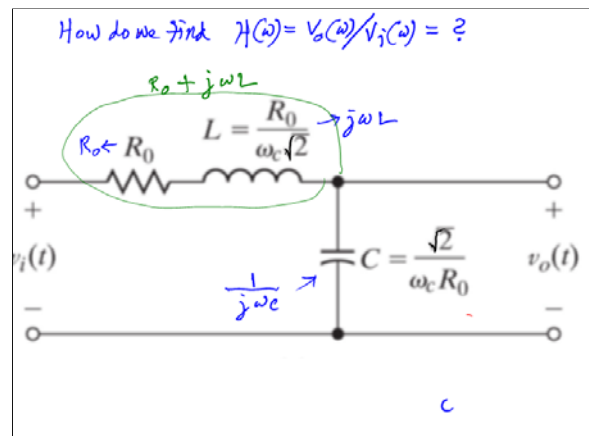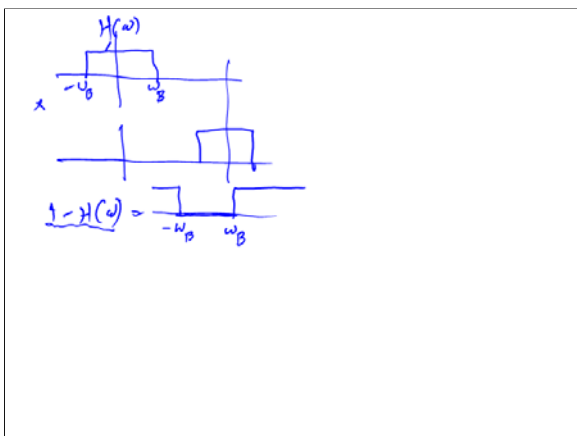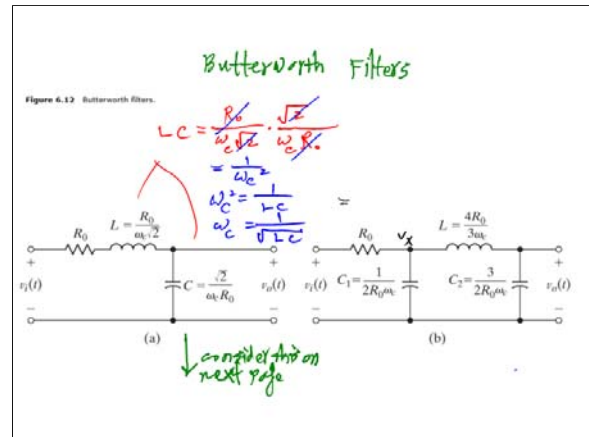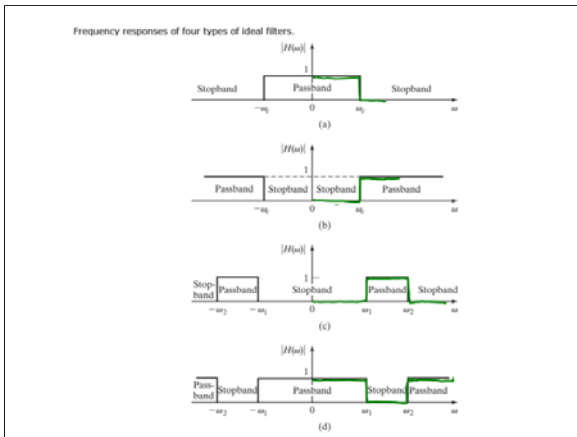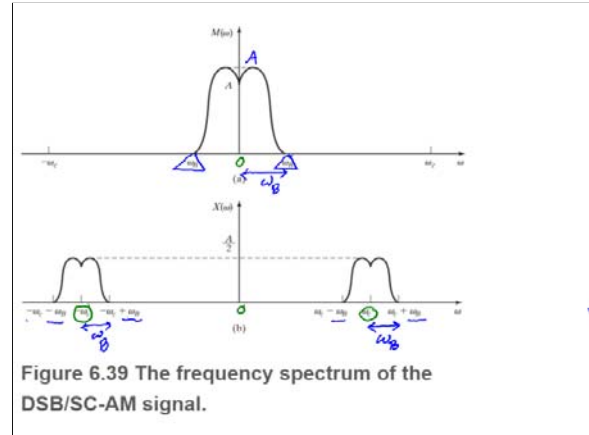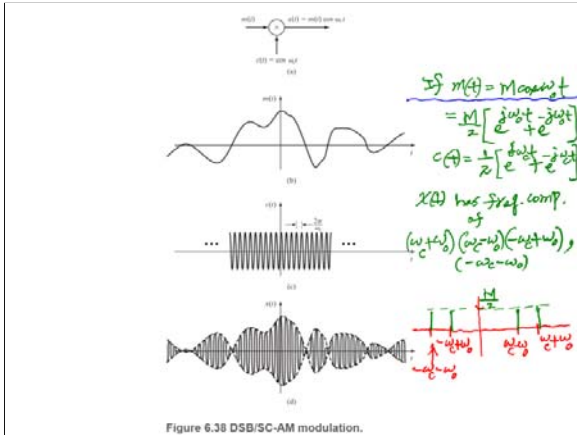
$$= \frac{\omega_c}{\pi} \text{sinc } \omega_c t$$



$V_i(t) = \text{input}$ $V_o(t) = \text{output}$
 $L = R \frac{d}{dt}$
 $C = \frac{1}{sC}$
 $H(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sC}}{(R + j\omega L) + \frac{1}{sC}}$
 $V_o(s) = V_i(s) \cdot \frac{1}{j\omega C} \cdot \frac{1}{(R + j\omega L) + \frac{1}{j\omega C}}$
 $\frac{V_o(s)}{V_i(s)} = \left[\frac{\frac{1}{j\omega C}}{(R + j\omega L) + \frac{1}{j\omega C}} \right] = \frac{1}{1 + j\omega RC + j\omega C(R + j\omega L)}$
 $H(\omega) \angle H(\omega) = \frac{1}{(1 - \omega^2 LC) + j\omega RC}$

$\left| \frac{1}{a + jb} \right| = \frac{1}{\sqrt{a^2 + b^2}}$
 $\angle \frac{1}{a + jb} = \angle 1 - \angle a + jb = -\angle a + jb = \frac{e^{j\theta_1}}{e^{j\theta_2}} = e^{j(\theta_1 - \theta_2)}$
 $\angle a + jb = \tan^{-1} \left(\frac{b}{a} \right)$
 $\theta = \tan^{-1} \left(\frac{2}{4} \right) = 36.9^\circ$
 $53.1^\circ = \tan^{-1} \frac{4}{3}$

$|H(\omega_x)| = \frac{|V_2(\omega_x)|}{|V_1(\omega_x)|} = A_2$

(a)

(b)

$H(\omega) = \frac{R}{R + j\omega L + 1/j\omega C} = \frac{j(R/L)\omega}{-\omega^2 + 1/LC + j(R/L)\omega}$
 $= \frac{j10^4\omega}{-\omega^2 + 10^8 + j10^4\omega}$
 $= \frac{1}{1 + j(\omega^2 - 10^8)/10^4\omega}$

The student wrote the transfer function in polar form as


$H(\omega) = |H(\omega)| e^{j\phi(\omega)}$

where

$\text{mag. } |H(\omega)| = \frac{1}{[1 + ((\omega^2 - 10^8)/10^4\omega)^2]^{1/2}}$

and

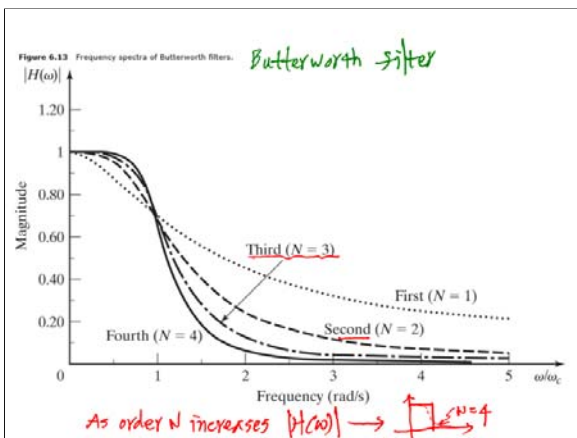$\text{phase } \phi(\omega) = -\tan^{-1} [(\omega^2 - 10^8)/10^4\omega]$



what happens when the freq. of $v_i(t)$ changes?
 $\left| \frac{V_2(\omega)}{V_1(\omega)} \right|$ vs. ω ?

(a) $|H(\omega)| = \left| \frac{V_2(\omega)}{V_1(\omega)} \right|$ vs ω

(b) $|H(\omega)|$ vs ω

(c) $|H(\omega)|$ vs ω



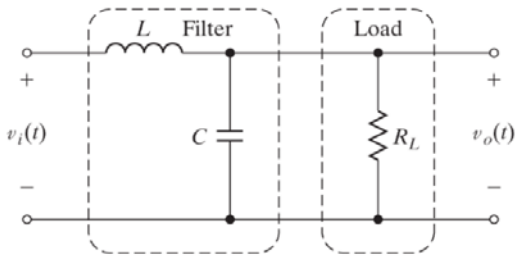
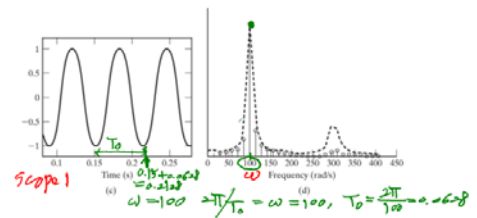
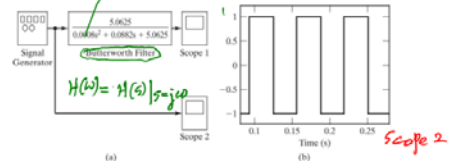
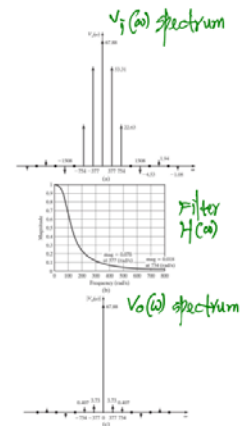
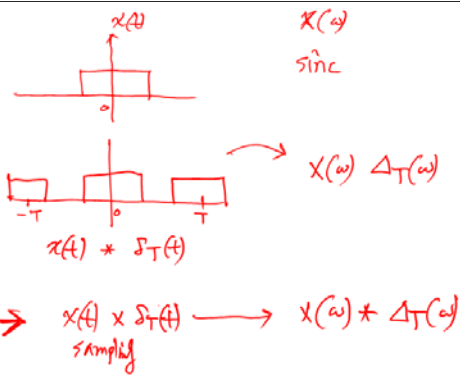
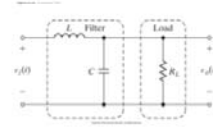
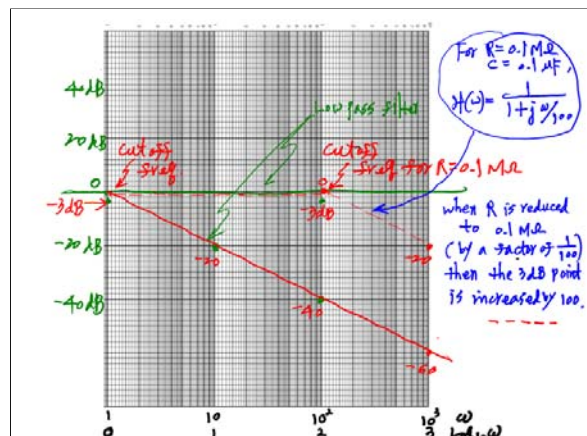
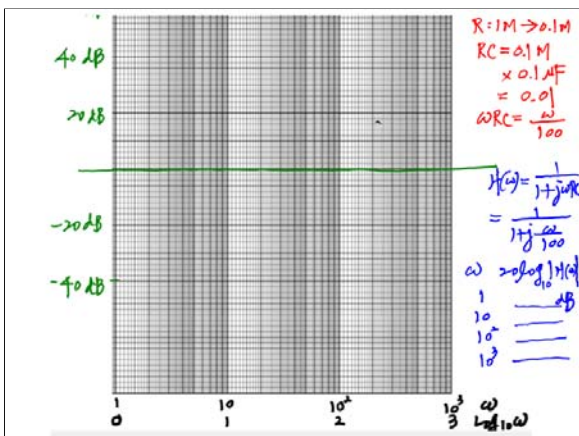
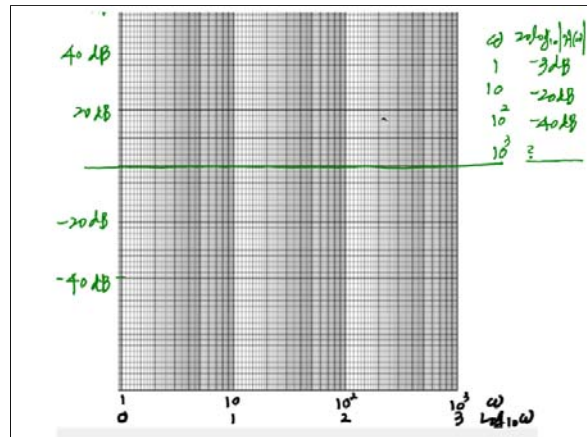
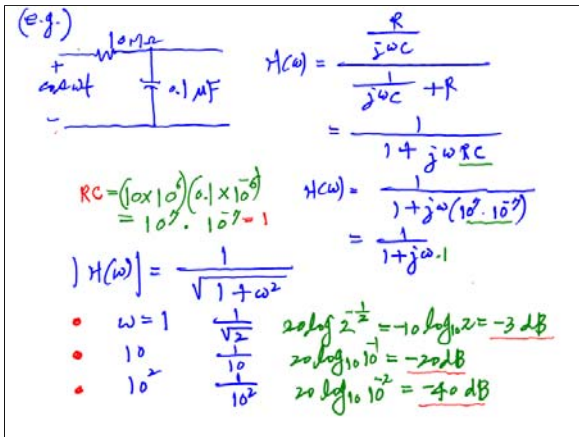


Figure 6.14 A practical filter. $\omega_0 = 2\pi f_0 = 2\pi(60) = 377$

$$V_1(\omega) = 53.31 \sum_{n=-\infty}^{\infty} \text{sinc}(n\pi/2) [\delta(\omega - (n+1)377) + \delta(\omega - (n-1)377)].$$

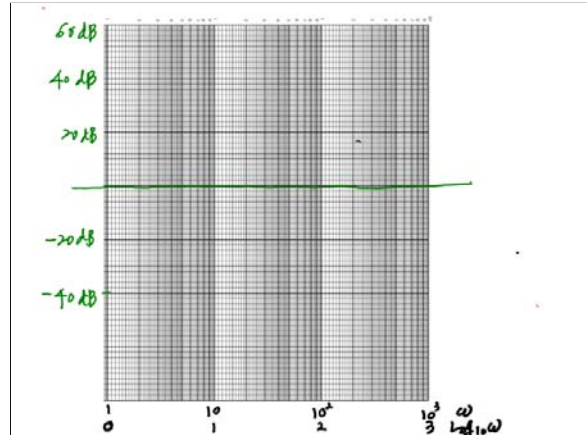How do we find $H(\omega) = V_o(\omega)/V_i(\omega)$ for the filter below?



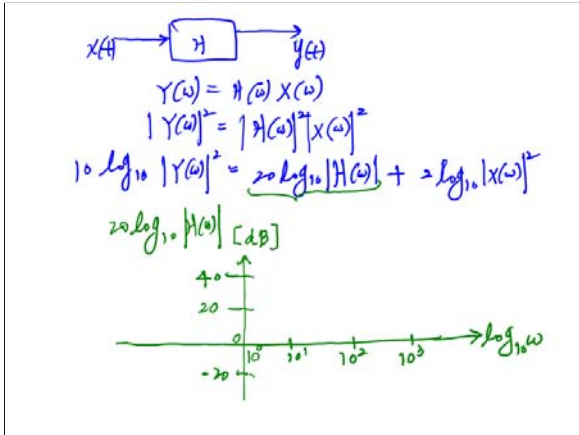

In general

$$H(\omega) = K \frac{(1 + \frac{\omega}{\omega_{z1}})(1 + \frac{\omega}{\omega_{z2}}) \dots (1 + \frac{\omega}{\omega_{zn}})}{(1 + \frac{\omega}{\omega_{p1}})(1 + \frac{\omega}{\omega_{p2}}) \dots (1 + \frac{\omega}{\omega_{pn}})}$$

$$20 \log_{10} |H(\omega)| = 20 \log_{10} |K| + \sum_{j=1}^m 20 \log_{10} |1 + \frac{\omega}{\omega_{zj}}| - \sum_{k=1}^n 20 \log_{10} |1 + \frac{\omega}{\omega_{pk}}|$$

Example

$$H(\omega) = 100 \frac{(1 + \frac{\omega}{100})}{(1 + \frac{\omega}{10})(1 + \frac{\omega}{1000})}$$

$$20 \log_{10} |H(\omega)| = 20 \log_{10} 100 + 20 \log_{10} |1 + \frac{\omega}{100}| - 20 \log_{10} |1 + \frac{\omega}{10}| - 20 \log_{10} |1 + \frac{\omega}{1000}|$$

(a)

$$v_2(t) = L \frac{di(t)}{dt}$$

$$v_R(t) = R i(t)$$

$$v_1(t) = L \frac{di(t)}{dt} + R i(t)$$

Solve for $i(t)$

$$V_1(\omega) = (j\omega L + R) I(\omega)$$

And

$$V_2(\omega) = j\omega L I(\omega)$$

$$\Rightarrow V_2(\omega) = \frac{j\omega L}{R + j\omega L} V_1(\omega)$$

(b)

$$V_2(\omega) = H(\omega) V_1(\omega)$$

$$|H(\omega)| = \frac{\omega L}{\sqrt{R^2 + (\omega L)^2}}$$

$$\angle H(\omega) = 90^\circ - \tan^{-1} \frac{\omega L}{R}$$

$$|V_2(\omega)| = |V_1(\omega)| |H(\omega)|$$

$$\angle V_2(\omega) = \angle V_1(\omega) + \angle H(\omega)$$

thus, $v_2(t) = |V_1(\omega)| |H(\omega)| \cos(\omega t + \phi_1 + \phi_2)$

For $v_1(t) = \cos \omega t$, $|V_1(\omega)| = 1$, $\phi_1 = 0^\circ$

and $v_2(t) = 1 \cdot |H(\omega)| \cos(\omega t + \phi_2)$

(a)

$$j\omega L = j\omega 10^2$$

$$\frac{1}{j\omega C} = \frac{1}{j\omega 10^{-4}}$$

$$j\omega L - j\frac{1}{\omega C} = j(\omega L - \frac{1}{\omega C})$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\omega_x = 2\pi f_x = 2\pi / T_x$$

(b)

$$\phi_x = \phi_1 + \phi_2$$

$$= \omega_x t + \frac{\phi_x}{\omega_x}$$

(c)

$$(t_1 - t_0) = \text{delay}$$

$$= -\phi_x / \omega_x$$

$$\Rightarrow \phi_x = -2\pi \frac{(t_1 - t_0)}{T_x}$$

$$\omega_x = \frac{2\pi}{T_x}$$

dB

Phase (degrees)

$0 \text{ dB at } \omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^2 \cdot 10^{-4}}} = \frac{1}{10^{-1}} = 10^1 = 10^4$

$\frac{1}{\sqrt{LC}} = 10^4$

$\frac{1}{\sqrt{LC}} = 10^4$