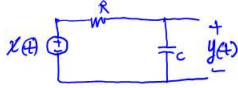


ECE 103 Lecture 26 Dec 3, 2018

Quiz P Average = 7.40  
 a<sub>0</sub> = 2.21

**Example 5-7: RC Circuit**

Determine  $v_{out}(t)$  when the circuit in Fig. 5-9(a) is excited by the voltage waveform shown in Fig. 5-9(b). The element values are  $R = 20 \text{ k}\Omega$  and  $C = 0.1 \text{ mF}$ .



Today Dec 3 (M)

Dec 5 (W) course review

Dec 7 (F) solving problems  
 by TA Azzam

For periodic  $x(t) = x(t + T)$ ,  $x(t) = \sum_{k=-\infty}^{\infty} C_k e^{+jk\omega_0 t}$   
 $\omega_0 = 2\pi/T_0$




$$C_k = a_k - jb_k$$

$$C_k = \frac{1}{T_0} \int_{T_0} x(t) e^{-jk\omega_0 t} dt$$

$$= \frac{1}{T_0} \int_{T_0} x(t) [a_k \cos k\omega_0 t - j \sin k\omega_0 t] dt$$

$$= \frac{1}{T_0} \int_{T_0} x(t) a_k \cos k\omega_0 t dt - j \frac{1}{T_0} \int_{T_0} x(t) \sin k\omega_0 t dt$$

$a_k$                        $b_k$

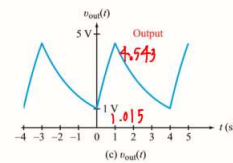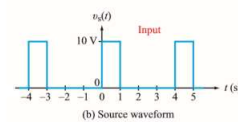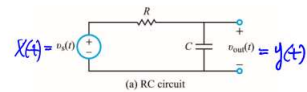

$RC = 20 \text{ k}\Omega \times 0.1 \text{ mF} = 2$

Figure 5-9: Circuit response to periodic pulses.

**Solution:**

**Step 1:** The period of  $v_s(t)$  is 4 s. Hence,  $\omega_0 = 2\pi/4 = \pi/2$  rad/s, and by Eq. (5.28), we have

$$a_0 = \frac{1}{T} \int_0^T v_s(t) dt = \frac{1}{4} \int_0^1 10 dt = 2.5 \text{ V},$$

$$a_n = \frac{2}{4} \int_0^1 10 \cos \frac{n\pi}{2} t dt = \frac{10}{n\pi} \sin \frac{n\pi}{2} \text{ V},$$

$$5 \int_0^1 \frac{2}{n\pi} d(\sin \frac{n\pi}{2})$$

$$b_n = \frac{2}{4} \int_0^1 10 \sin \frac{n\pi}{2} t dt = \frac{10}{n\pi} (1 - \cos \frac{n\pi}{2}) \text{ V},$$

and

$$\hat{c}_n = c_n / \phi_n = a_n - jb_n = \frac{10}{n\pi} \left[ \sin \frac{n\pi}{2} - j(1 - \cos \frac{n\pi}{2}) \right].$$

The values of  $c_n / \phi_n$  for the first four terms are

$$\hat{c}_1 = c_1 / \phi_1 = \frac{10\sqrt{2}}{\pi} / -45^\circ,$$

$$\hat{c}_2 = c_2 / \phi_2 = \frac{10}{\pi} / -90^\circ,$$

$$\hat{c}_3 = c_3 / \phi_3 = \frac{10\sqrt{2}}{3\pi} / -135^\circ,$$

and  $\hat{c}_n = c_n \delta(\omega) = 0$ .

Step 2: In the phasor domain, the impedance of a capacitor is  $Z_c = 1/(j\omega C)$ . By voltage division, the generic phasor-domain transfer function of the circuit is

$$H(\omega) = \frac{V_o}{V_s} = \frac{1}{1 + j\omega RC} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} e^{-j \tan^{-1}(\omega RC)}$$

where we used  $RC = 2 \times 10^3 \times 10^{-4} = 2 \text{ s}$ .

Step 3: The time-domain output voltage is

$$v_o(t) = 2.5 \sum_{n=-\infty}^{\infty} \Re \left\{ \hat{c}_n \frac{1}{\sqrt{1 + 4\omega_n^2}} e^{j(\omega_n t - \tan^{-1}(2\omega_n))} \right\}$$

Using the values of  $c_n \delta(\omega_n)$  determined earlier for the first four terms and replacing  $\omega_n$  with its numerical value of  $\pi/2 \text{ rad/s}$ , the expression becomes

$$v_o(t) = 2.5 \left[ \frac{10\sqrt{2}}{\pi\sqrt{1+4}} \cos\left[\frac{\pi t}{2} - 45^\circ - \tan^{-1}(2\pi)\right] + \frac{10}{\pi\sqrt{1+16}} \cos[\pi t - 90^\circ - \tan^{-1}(4\pi)] + \frac{10\sqrt{2}}{3\pi\sqrt{1+64}} \cos\left[\frac{3\pi t}{2} - 135^\circ - \tan^{-1}(6\pi)\right] + \dots \right]$$

$$= 2.5 + 1.37 \cos\left[\frac{\pi t}{2} - 117^\circ\right] + 0.5 \cos(\pi t - 171^\circ) + 0.16 \cos(2\pi t - 141^\circ) \dots$$

$$x(t) = \sum_{n=-\infty}^{\infty} \hat{c}_n e^{j n \omega_0 t}$$

$$X(\omega) = \sum_{n=-\infty}^{\infty} \hat{c}_n 2\pi \delta(\omega - n\omega_0)$$

$$V_o(\omega) = X(\omega) H(\omega)$$

$$= \sum_{n=-\infty}^{\infty} \hat{c}_n 2\pi H(n\omega_0) \delta(\omega - n\omega_0)$$

$$v_o(t) = \sum_{n=-\infty}^{\infty} c_n e^{j n \omega_0 t} |H(n\omega_0)| e^{j \angle H(n\omega_0)}$$

$$= c_0 |H(0)| + \sum_{n=1}^{\infty} 2c_n |H(n\omega_0)| \cos(n\omega_0 t + \angle H(n\omega_0))$$

$R = 20 \text{ k}\Omega$   
 $C = 0.1 \text{ mF}$

$\hat{v}_s(t) = RC \frac{dv_o(t)}{dt} + v_o(t)$   
 $\hat{v}_s(\omega) = RC [j\omega v_o(\omega) - v_o(0)] + v_o(\omega)$   
 $\hat{v}_s(\omega) + RC v_o(\omega) = (RCs + 1) v_o(\omega)$   
 $v_o(\omega) = \frac{\hat{v}_s(\omega) + RC v_o(0)}{RCs + 1}$   
 $= \frac{\hat{v}_s(\omega) + v_o(0)}{s + \frac{1}{RC}}$   
 $= \frac{1}{RC} \hat{v}_s(\omega) \frac{1}{s + \frac{1}{RC}} + v_o(0) \frac{1}{s + \frac{1}{RC}}$

For  $RC = 20 \times 10^3 \times 0.1 \times 10^{-3} = 2$ ,  
For  $0 < t < 1$ ,  $v_o(\omega) = \frac{1}{2} \frac{10}{s} - \frac{1}{s + 0.5} + v_o(0) \frac{1}{s + 0.5}$   
 $v_o(t) = [10(1 - e^{-0.5t}) + v_o(0)(e^{-0.5t} - 1)] u(t)$   
At  $t = 4$ ,  $v_o(4) = [10(1 - e^{-0.5}) + v_o(0)(e^{-0.5} - 1)] e^{-2} = v_o(2)$

$$\frac{1}{2} \frac{10}{s} \frac{1}{s + 0.5} = 5 \left[ \frac{2}{s} + \frac{-2}{s + 0.5} \right]$$

$$\frac{1}{s(s + 0.5)} = \frac{A}{s} + \frac{B}{s + 0.5}$$

$$A = \frac{1}{s(s + 0.5)} \times s \Big|_{s=0} = \frac{1}{s + 0.5} \Big|_{s=0} = -2$$


$$B = \frac{1}{s(s + 0.5)} (s + 0.5) \Big|_{s=-0.5} = -2$$

$$\rightarrow 10 \left[ \frac{1}{s} - \frac{1}{s + 0.5} \right]$$

$v_o(t) = [10(1 - e^{-0.5t}) + v_o(0) e^{-0.5t}] - 1.5 = v_o(0)$   
 $10(1 - e^{-0.5}) = v_o(0)(e^{-1.5} - e^{-0.5})$   
 $v_o(0) = \frac{10(1 - e^{-0.5})}{e^{-1.5} - e^{-0.5}} = 1.015$   
 $v_o(1) = v_o(0) e^{-0.5} + 10(1 - e^{-0.5}) = 0.6156 + 10 \times 0.9347 = 4.550$

6.3 For the circuit shown in Fig. P6.3, determine (a) the transfer function  $H = V_o/V_i$ , and (b) the frequency  $\omega_0$  at which  $H$  is purely real.

Figure P6.3: Circuit for Problem 6.3.

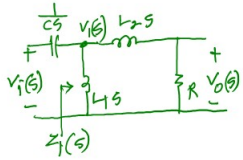

$$Z_1(s) = L_1 s \parallel (L_2 s + R) = \frac{L_1 s (L_2 s + R)}{L_1 s + (L_2 s + R)}$$

$$= \frac{L_1 L_2 s^2 + L_1 R s}{(L_1 + L_2) s + R}$$

$$V_1(s) = V_i(s) \frac{Z_1(s)}{\frac{1}{cs} + Z_1(s)}$$

$$= V_i(s) \frac{Z_1(s) cs}{1 + Z_1(s) cs} = V_i(s) \frac{(L_1 L_2 s^2 + L_1 R s) cs}{(L_1 + L_2) s + R + (L_1 L_2 s^2 + L_1 R s) cs}$$

$$V_0(s) = V_1(s) \frac{R}{L_2 s + R}$$

$$= V_i(s) \frac{(L_1 L_2 s^2 + L_1 R s) cs}{(L_1 + L_2) s + R + (L_1 L_2 s^2 + L_1 R s) cs} \frac{R}{L_2 s + R}$$

$$\frac{V_0(s)}{V_i(s)} = \frac{(L_1 L_2 s^2 + L_1 R s) R cs}{[(L_1 + L_2) s + R + (L_1 L_2 s^2 + L_1 R s) cs] (L_2 s + R)}$$

$$= \frac{L_1 R cs^2 (L_2 s + R)}{(L_1 L_2 s^2 + L_1 R cs + (L_1 + L_2) s + R) (L_2 s + R)}$$

$$H(\omega) = \frac{L_1 R c (-\omega^2)}{j\omega(L_1 + L_2 - L_1 L_2 \omega^2) - L_1 R c \omega^2 + R}$$

denominator

$$j\omega(L_1 + L_2 - L_1 L_2 \omega^2) - L_1 R c \omega^2 + R$$

real when  $\omega = \sqrt{\frac{L_1 + L_2}{L_1 L_2}}$

$$H(\omega) = \frac{L_1 R c (-\omega^2)}{j\omega(L_1 + L_2 - L_1 L_2 \omega^2) - L_1 R c \omega^2 + R}$$

$$\angle H(\omega) = \angle \text{numerator} - \angle \text{denominator}$$

$$\angle \text{numerator} = \angle -(L_1 R c \omega^2) = 180^\circ$$

$$\angle \text{denominator} = \tan^{-1} \left[ \frac{(L_1 + L_2 - L_1 L_2 \omega^2)}{R_1 - L_1 R c \omega^2} \right]$$

$$\angle H(\omega) = 90^\circ \quad \omega = ?$$

$$\Rightarrow \tan^{-1} \left[ \frac{L_1 + L_2 - L_1 L_2 \omega^2}{R_1 - L_1 R c \omega^2} \right] = 90^\circ$$

$$\omega = \sqrt{\frac{R_1 - \epsilon}{L_1 R c}} \quad \text{for small } \epsilon$$

$$\epsilon = R_1 - L_1 R c \omega^2 \quad \frac{\epsilon - R_1}{-L_1 R c} = \omega^2$$